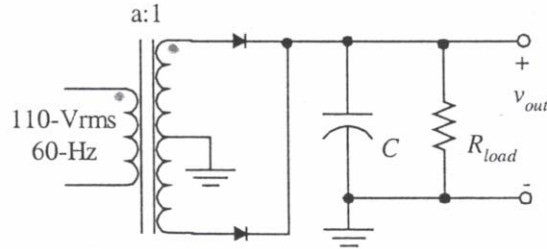




**Show all work. Clearly indicate final answer(s).**

- (20 points) A particular diode has a reverse saturation current of  $0.2\mu\text{A}$ ,  $n=1.6$ , and  $V_T=26\text{mV}$ . Determine the diode current when the voltage across the diode is  $0.4\text{V}$ . Also determine the forward resistance of the diode at this operating point. Hint: Assume zero contact resistance.

- (40 points) Determine the capacitor size for the circuit shown to the right when  $a=6$  and  $R_{\text{load}}=100\Omega$ . The minimum voltage to the load must not drop by more than 20%. Consider the diodes and transformer ideal.




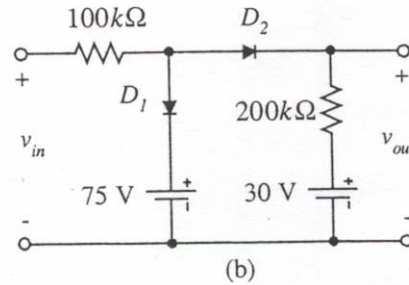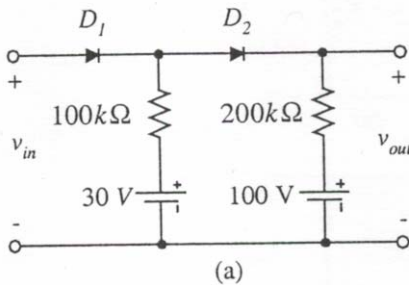- (40 points)
  - The input voltage to the clipper circuit in figure (a) varies linearly from 0 to 150V. Sketch the output voltage,  $v_{\text{out}}$ , on the same time plot as the input. Assume the diodes are ideal.
  - Repeat part (a) for the circuit in figure (b).



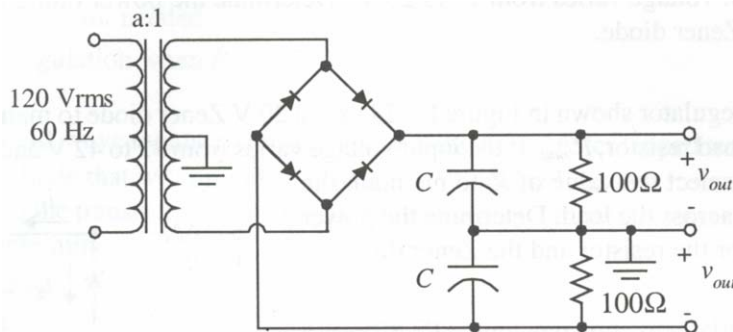**EXTRA CREDIT (20 points max):**

An integrated circuit requires plus and minus voltages for their operation. Using the circuit to the right, determine the transformer winding ratio and the capacitor size needed to get a maximum of 14V and a minimum of 12V at the output when the input is 120Vrms 60Hz,  $V_{\text{ON}}=0.7\text{V}$  for each of the diodes and  $R_f=0$ . Ignore transformer loss.



**(HOPEFULLY!) USEFUL STUFF**

$$v_{out,avg} = \frac{1}{T} \int_0^T v_{out}(t) dt = \frac{1}{T} \int_0^{T/2} V_0 \sin \frac{2\pi t}{T} dt + \frac{1}{T} \int_{T/2}^T 0 dt = \frac{V_0}{\pi} + 0 \approx 0.318V_0$$

$$R_i = \frac{V_{smin} - V_z}{I_{Lmax} + I_{zmin}} = \frac{V_{smax} - V_z}{I_{Lmin} + I_{zmax}}$$

$k_T = -2.0 \text{ mV/}^\circ\text{C}$  for Si,  $-2.5 \text{ mV/}^\circ\text{C}$  for Ge

$$i_D = I_0 (e^{\frac{v_D}{nV_T}} - 1)$$

26mV@room temperature

$$\% \text{ reg} = \frac{V_{outmax} - V_{outmin}}{V_{outnominal}} * 100$$

$$r_d = \frac{nV_T}{i_D}$$

$$C = \frac{V_{max}}{\Delta V f_p R_L}$$

$$C_F = \frac{V_{smax} - V_z}{\Delta V f_p R_i}$$

$$V_{ON}(T_{New}) - V_{ON}(T_{room}) = k_T (T_{New} - T_{room})$$

$$I_0(atT_2) = I_0(atT_1) e^{k_i(T_2 - T_1)}$$

$$J = q(p\mu_p + n\mu_n)E$$

$$R = \frac{\rho L}{A} = \frac{L}{\sigma A}$$

$$I_{zmax} = \frac{I_{Lmin}(V_z - V_{smin}) + I_{Lmax}(V_{smax} - V_z)}{V_{smin} - 0.9V_z - 0.1V_{smax}}$$

1)  
P3.11

Given:  $I_0 = 0.24 \mu\text{A}$

$n = 1.6$

$V_T = 26 \text{ mV}$

Want  $i_D$ , when  $v_D = 0.4 \text{ V}$


$R_F$

$$i_D = I_0 \left( e^{\frac{v_D}{nV_T}} - 1 \right) = (2 \times 10^{-7}) e^{\left( \frac{0.4}{(1.6)(0.026)} \right) - 1}$$

$$i_D \approx 3 \text{ mA}$$

$$R_F \approx r_D = \frac{nV_T}{i_D} = \frac{(1.6)(26 \text{ mV})}{3 \text{ mA}} = 13.9 \Omega$$

2)  
P3.23

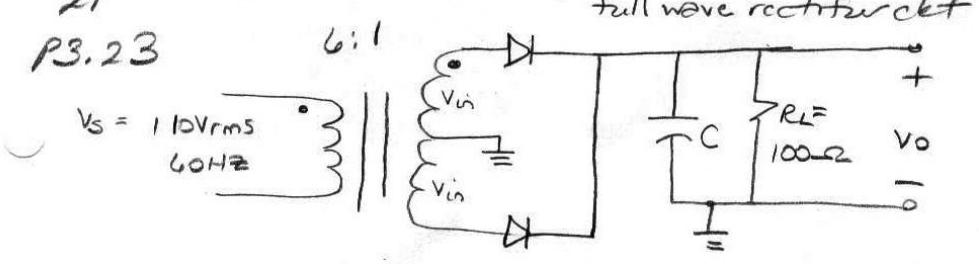

$C = ?$   
 Given: Ideal diode ( $V_{on} = 0, R_f = 0, R_r = \infty$ )  
 Ideal transformer

*for 100% ripple*  
 $V_{inmin} \geq 0.8 V_{inmax}$  (can't drop by more than 20%)

$$V_{speak} = 110\sqrt{2} = 155.6 \text{ V}_{peak}$$

$$V_{inpeak} = \frac{155.6}{(6)(2)} \approx 13 \text{ V}_{peak}$$

↑ center tap

$$\Delta V_{max} = (0.2)V_{inmax} = (0.2)(13) = 2.6 \text{ V}$$


$$V_{inmin} = (0.8)(13) = 10.4 \text{ V}$$

(not a necessary calculation - could use  $\Delta V = V_{max} - V_{min} = 2.6 \text{ V}$ )



$$C = \frac{V_{inmax}}{\Delta V_{max} f_p R_L} = \frac{(13)}{(2.6)(120)(100)} \approx \frac{417 \mu\text{F}}{32}$$

3) ideal diodes  $\Rightarrow V_{on}=0, R_f=0, R_r=\infty$


P3.41

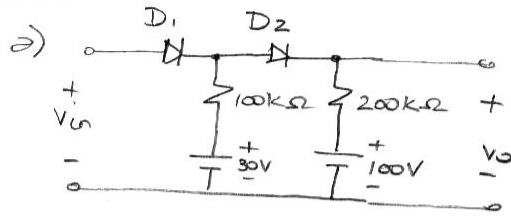

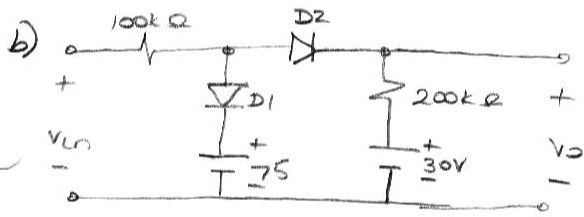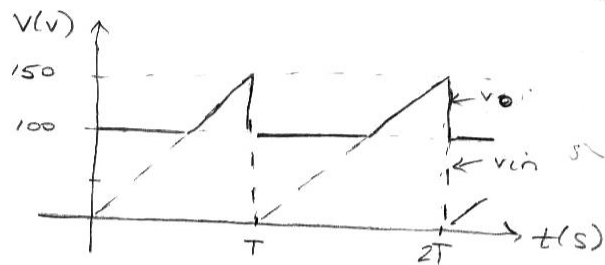$\forall V_{in} < 30V, D_1 \text{ off}, D_2 \text{ off}, V_o = 100V$   
 $\forall 30 \leq V_{in} < 100V, D_1 \text{ on}, D_2 \text{ off}, V_o = 100V$   
 $\forall V_{in} \geq 100V, D_1 \text{ on}, D_2 \text{ on}, V_o = V_{in}$   
 (everything is in parallel if diodes are ideal)



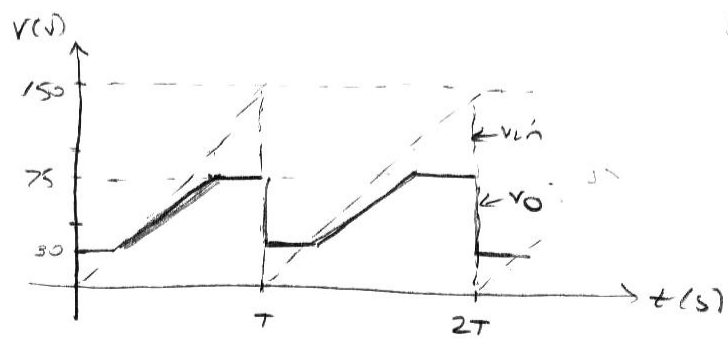$\forall V_{in} < 30V, D_1 \text{ off}, D_2 \text{ off}, V_o = 30V$   
 $\forall 30 < V_{in} < 75, D_1 \text{ off}, D_2 \text{ on}$   
 $V_o = 30 + \left(\frac{V_{in}-30}{300k}\right)(200k)$   
 $V_o = 10 + \frac{2}{3}V_{in}$   
 $\text{max } V_o = 75V \text{ (when } D_1 \text{ on)}$   
 $V_o = 75 @ 75 = 10 + \frac{2}{3}V_{in}$   
 $\forall V_{in} = \frac{3}{2}(75-10) = 97.5V$



$V_{in}$	$V_o$
$< 30$	30
50	43.3
75	60
$> 97.5$	75

EC P325

voltage needed @ secondary:

$$2(V_{\text{max}} + 2V_{\text{on}}) = 2(14 + 1.4) = 30.8V_{\text{(peak)}}$$

↑  
center tap      ↑  
2 diodes on each path

$$V_{\text{rms}} = 120\sqrt{2} \approx 169.7V$$

$$a = \frac{169.7}{30.8} \approx 5.5 \quad (\text{w: } 5.5:1, \text{ or } 11:2)$$

$$\Delta V = (14 - 12) = 2V$$

$$f_p = 120 \text{ Hz (full wave rectifier)}$$

$$C = \frac{V_{\text{max}}}{\Delta V f_p R_L} = \frac{14}{2(120)(100)} = \underline{\underline{583\mu\text{F}}}$$