
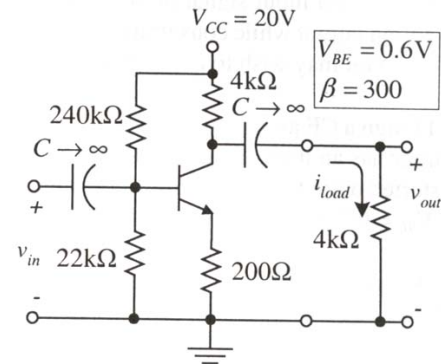


Show all work. Clearly indicate final answer(s).

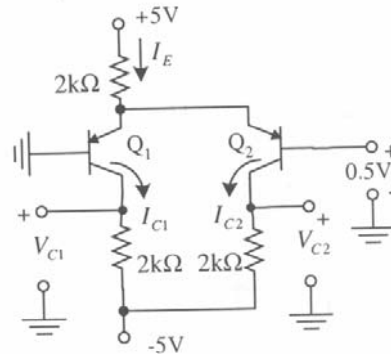
1. (40 points) Analyze the circuit shown to the right and determine the following:
 - a. I_{CQ} and V_{CEQ}
 - b. Maximum undistorted output voltage swing
 - c. Power supplied from power supply
 - d. Voltage gain
 - e. Load lines (sketch)



2. (30 points) Using simple analytical techniques for the circuit shown to the right, determine the values of I_E , V_E , I_{C1} , I_{C2} , V_{C1} and V_{C2} . Use $V_{BE} = -0.7V$ as the condition for the transistor(s) to be on.




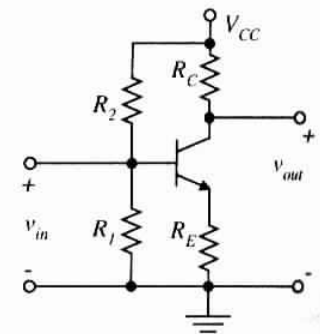3. (30 points) For the amplifier shown to the right, $V_{BE} = 0.6V$, $V_{CC} = 12V$, $\beta = 300$, $P_{load(max\ average)} = 100mW$, and $A_V = -10V/V$. Design for maximum swing and determine R_1 and R_2 . How much power is dissipated in the transistor?




Extra Credit (30 points maximum)

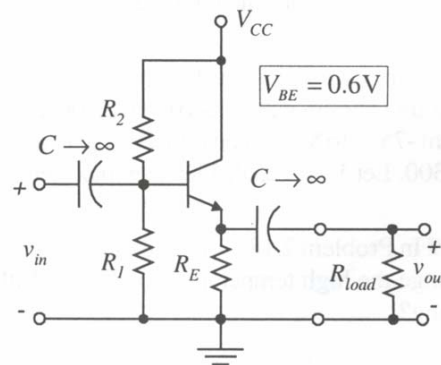Design an EF (CC) amplifier to drive an 8Ω load. Set the current gain, $A_i = 10$ A/A. Determine the peak-to-peak output voltage swing if the temperature rises to $75^\circ C$. Assume $I_{CBO}(25^\circ C) = 0.008\mu A$, $V_{BE} = 0.6V$, $V_{CC} = 24V$ and β varies over the range from 60 to 100. Hint: design for maximum swing at $25^\circ C$.



P1
P5.15

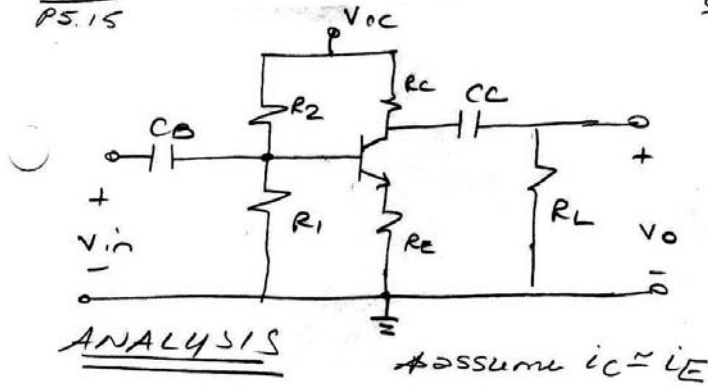

Given: $C_B = C_C \rightarrow \infty$
 $R_1 = 22\text{k}\Omega$
 $R_2 = 240\text{k}\Omega$
 $R_C = 4\text{k}\Omega$
 $R_E = 200\Omega$
 $R_L = 4\text{k}\Omega$
 $V_{BE} = 0.6\text{V}$
 $V_{CC} = 20\text{V}$
 $\beta = 300$

1/2

ANALYSIS

Assume $I_C = I_E$

a) $I_{CQ} + V_{CEQ}$

$$R_B = R_1 \parallel R_2 = (22\text{k}) \parallel (240\text{k}) \approx 20.2\text{k}\Omega$$

$$V_{BB} = \frac{R_2 V_{CC}}{R_1 + R_2} = \frac{(22\text{k})(20)}{22\text{k} + 240\text{k}} \approx 1.68\text{V}$$

$$I_{CQ} = \frac{V_{BB} - V_{BE}}{R_B/\beta + R_E} = \frac{1.68 - 0.6}{20.2\text{k}/300 + 0.2\text{k}} \approx \underline{4.04\text{mA}}$$

$$V_{CEQ} = V_{CC} - I_{CQ} R_{DC} = 20 - (4.04\text{mA})(4.2\text{k}) = \underline{3.03\text{V}}$$

\uparrow
 $R_C + R_E$

b) max V_{opp} (undistorted)

$$V'_{CC} = V_{CEQ} + I_{CQ} R_{AC} = 3.03 + (4.04\text{mA})(2.2\text{k}) = 11.92\text{V}$$

\uparrow
 $R_C \parallel R_L + R_E$

$$I_{CC} = \frac{V'_{CC}}{R_{AC}} = \frac{11.92}{2.2\text{k}} = 5.42\text{mA}$$

$\therefore I_{CQ}$ in upper half of ac ll

$$V_{opp} = 2[0.95I_{CC} - I_{CQ}] R_{Loff}$$

\uparrow
 $R_C \parallel R_L$

$$= 2[(0.95)(5.42\text{mA}) - (4.04\text{mA})](2\text{k})$$

$$\underline{V_{opp} = 4.44\text{V}}$$

P1(cont)

2/2


$$c) P_{dc} = \frac{V_{cc}^2}{R_1 + R_2} + V_{CEQ} I_{CQ} + I_{CQ}^2 (R_C + R_E)$$
$$= \frac{20^2}{262k} + (3.03)(4.04m) + (4.04m)^2 (7.2k)$$

$$\approx (1.53 + 12.24 + 68.55)m$$

$$P_{dc} \approx 82.32mW$$

$$d) A_v = -\frac{R_C \parallel R_L}{r_e + R_E} \quad ; \quad r_e = \frac{V_T}{I_{CQ}} = \frac{26m}{4.04m} = 6.44\Omega$$

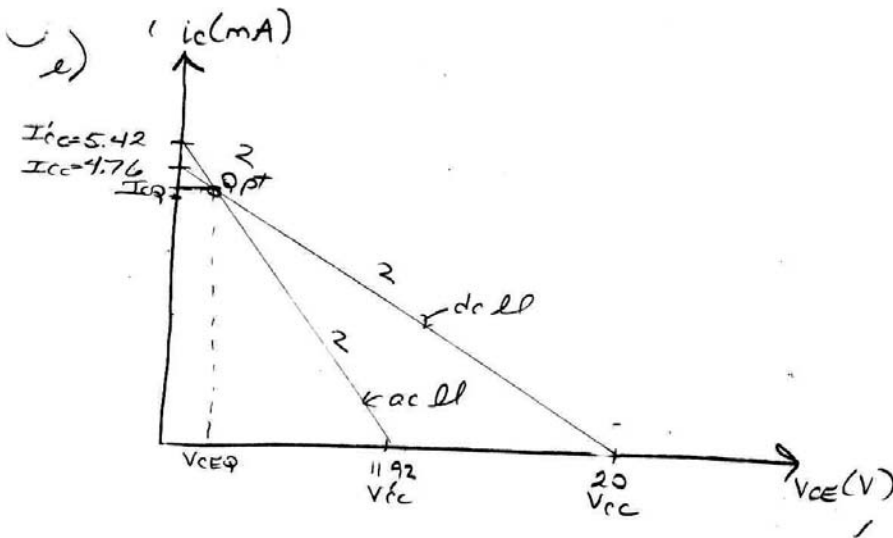
$$A_v = -\frac{4k \parallel 4k}{6.44 + 200} = -9.69V/V$$



$$I_{cc} = \frac{V_{cc}}{R_{dc}} = \frac{20}{4.2k} = 4.76mA$$

P2

P5.52

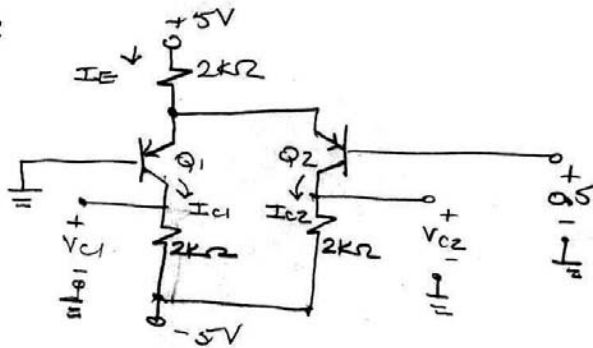

$$V_{BE} = -0.7V$$

$$V_{B1} = 0 + V_{BE} = -0.7V \therefore V_{E1} = 0.7V = V_{E2}$$

$$\therefore I_E = \frac{5 - 0.7}{2K} = \underline{2.15mA}$$

$$Q_1 \text{ on, } I_C > 0$$

$$V_{B2} = 0.5V + V_{E1} = V_{E2} = 0.7V$$

$$\therefore V_{BE2} = 0.5 - 0.7 = -0.2V, < -0.7V \text{ so } Q_2 \text{ off}$$

$$Q_2 \text{ off, } I_{C2} = 0$$


$$\therefore I_{C1} = I_E = 2.15mA$$

$$I_{C2} = 0$$

$$\therefore V_{C1} = -5 + I_{C1}(2K) = -5 + (2.15m)(2K) = \underline{-0.7V}$$

$$\therefore V_{C2} = \underline{-5V}$$

P3
PS.5

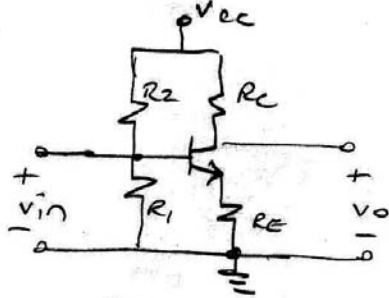

Given: $V_{BE} = 0.6V$
 $V_{CC} = 12V$
 $\beta = 300$
 $P_{load(max\ avg)} = 100mW$
 $A_v = -10V/V$

Find: $R_1, R_2, R_{in}, A_i, P_{tran}$

ER Amp: $A_v = -\frac{R_C \parallel R_L}{r_e + R_E}$ ①

no R_L given ($R_L = \infty$)
 so R_C acts as load

$P_{load} = \frac{1}{2} I_{CQ}^2 R_C$ ②

$I_{CQ} = \frac{V_{CC}}{R_A \parallel R_C} = \frac{V_{CC}}{(R_E + R_C) + (R_E + R_C)} = \frac{V_{CC}}{2(R_E + R_C)}$ ③

from 1, (assume $r_e \ll R_E$) $-10 = -\frac{R_C}{R_E}$; $R_C = 10R_E$

\rightarrow ③: $I_{CQ} = \frac{12}{2(11R_E)} = \frac{6}{11R_E}$

\rightarrow ②: $100m = \frac{1}{2} \left(\frac{6}{11R_E}\right)^2 (10R_E) = \frac{1.49}{R_E}$

$R_E = \frac{1.49}{0.1} = 14.9\Omega$; $R_C = 149\Omega$, $I_{CQ} = 36.6\mu A$

$R_B = 0.1\beta R_E = (0.1)(300)(14.9) = 447\Omega$

$V_{BB} = V_{BE} + I_{CQ} \left(\frac{R_B}{\beta} + R_E\right) = 0.6 + (36.6\mu A) \left(\frac{447}{300} + 14.9\right) = 1.2V$


$R_1 = \frac{R_B}{1 - V_{BB}/V_{CC}} = \frac{447}{1 - 1.2/12} = 497\Omega$

$R_2 = \frac{R_B V_{CC}}{V_{BB}} = \frac{(447)(12)}{1.2} = 4.47k\Omega$

$V_{CEQ} = V_{CC} - I_{CQ} R_{DC} = 12 - (36.6\mu A)(149 + 14.9) = 6V$

$P_{tran} = I_{CQ} V_{CEQ} = (36.6\mu A)(6) \approx 220mW$

10/2/18

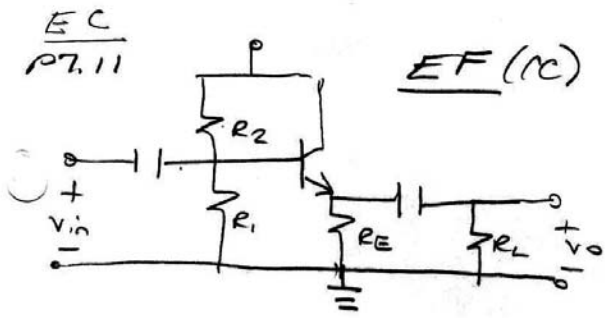

Y2

Given: $R_L = 8\Omega$
 $A_i = 10^4/A$
 $I_{CBO}(25^\circ C) = 0.0084A$
 $V_{BE} = 0.6V$
 $V_{CC} = 24V$
 $60 \leq \beta \leq 100$

Want:
 a) Design amp for max swing
 b) V_{opp} @ $75^\circ C$

* assume β large enough
 so that $i_C \approx i_E$

$$A_i = \frac{R_B}{R_B/\beta + r_c + (R_E \parallel R_L)} \frac{R_E}{R_E + R_L}$$

Let $R_E = R_L = 8\Omega$; $R_E \parallel R_L = 4\Omega$
 assume r_c negligible

use $\beta = \beta_{avg} = \frac{60+100}{2} = 80$

$$A_i = 10 = \frac{R_B}{R_B/80 + 4} \frac{8}{16} \Rightarrow 20 \left(\frac{R_B}{80} + 4 \right) = R_B \Rightarrow$$

$$80 = R_B \left(1 - \frac{1}{4} \right) \Rightarrow R_B = \frac{80}{0.75} \approx 107\Omega$$

Design for max swing: $I_{CQ} = \frac{V_{CC}}{R_C + R_E} = \frac{V_{CC}}{(R_E \parallel R_L) + R_E}$

$$I_{CQ} = \frac{24}{4 + 8} = 2A ; r_c = \frac{V_T}{I_{CQ}} = \frac{26m}{2} = 13m\Omega$$

↑ assumption ok

$$V_{BB} = V_{BE} + I_{CQ} \left(\frac{R_B}{\beta} + R_E \right) = 0.6 + (2) \left(\frac{107}{80} + 8 \right) = 19.3V$$

$$R_1 = \frac{R_B}{1 - V_{BB}/V_{CC}} = \frac{(107)}{1 - 19.3/24} = \underline{\underline{546\Omega}}$$

$$R_2 = \frac{R_B V_{CC}}{V_{BB}} = \frac{(107)(24)}{19.3} = \underline{\underline{133\Omega}}$$

b) $\Delta T = T_2 - T_1 = 75 - 25 = 50^\circ C$

$k \Delta \beta = 100 - 60 = 40$

$\Delta V_{CC} = 0$ (given as constant)

$k \Delta V_{BE} = k_T (T_2 - T_1) = (-2mV/^\circ C)(50^\circ C) = -100mV$

$k \Delta I_{CBO} = I_{CBO}(T_1) \left[e^{\frac{k_i(T_2 - T_1)}{e}} - 1 \right] = (0.008\mu A) \left[e^{(0.15 \times 50)} - 1 \right] \approx 14.5\mu A$

$\delta V = \frac{-1}{R_E + R_B/\beta} = \frac{-1}{8 + 107/80} = -0.107$

$\delta I = \frac{\beta}{1 + \beta R_E/R_B} = \frac{80}{1 + \frac{(80)(8)}{107}} = 11.46$

$\delta \beta = \frac{R_B (V_{BB} - V_{BE})}{(\beta R_E)^2} = \frac{(107)(19.3 - 0.6)}{((80)(8))^2} = 4.89 \times 10^{-3}$

$\Delta I_C = \delta V \Delta V_{BE} + \delta I \Delta I_{CBO} + \delta \beta \Delta \beta$ ($\delta V_{CC} \Delta V_{CC} = 0$)

$\Delta I_C = (-0.107)(-100m) + (11.46)(14.5\mu) + (4.89 \times 10^{-3})(40)$
 ↑ positive since net of 1st 2 terms is positive

$\Delta I_C = 10.7m + 0.17m + 195.6m \approx 206.5m A$

$I_{CQ}(75^\circ C) = I_{CQ}(25^\circ C) + \Delta I_C = 2 + 206.5m \approx 2.21A$

$V_{CEQ}(75^\circ C) = V_{CC} - I_{CQ} R_{DC} = 24 - (2.21)(8) = 6.32V$

$V_{CC}(75^\circ C) = V_{CEQ} + I_{CQ} R_{AC} = 6.32 + (2.21)(4) = 15.16V$

$I_{CC}(75^\circ C) = \frac{V_{CC}}{R_{AC}} = \frac{15.16}{4} = 3.79A \therefore I_{CQ}$ in upper half

$V_{app} = 2 [0.95 I_{CC} - I_{CQ}] R_{LAF} = 2 [(0.95)(3.79) - 2.21](4) \approx 11.1V_{pp}$
 @ 75°C