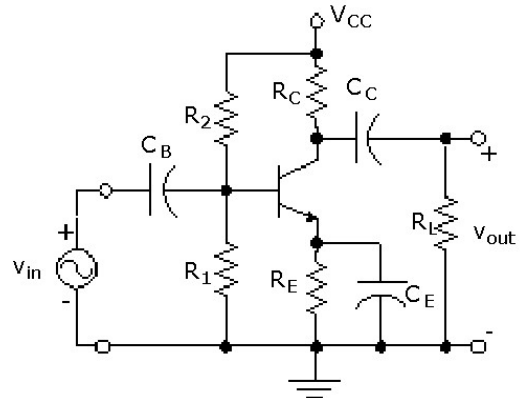



Show all work. Clearly indicate final answer(s).

Cheatsheet must be turned in with test or a zero will be given for the *entire* test!


1. (40 pts) For the circuit to the right, if $R_1=1.5k\Omega$, $R_2=7k\Omega$, $R_E=100\Omega$, $R_C=R_L=1k\Omega$, $\beta=180$, $V_{BE}=0.7V$, $V_{CC}=5V$ and all capacitors are infinite and ideal, determine:
 - a. the Q-point;
 - b. V_{opp} ;
 - c. $P_{out(ac)}$;
 - d. dc power delivered by the source.



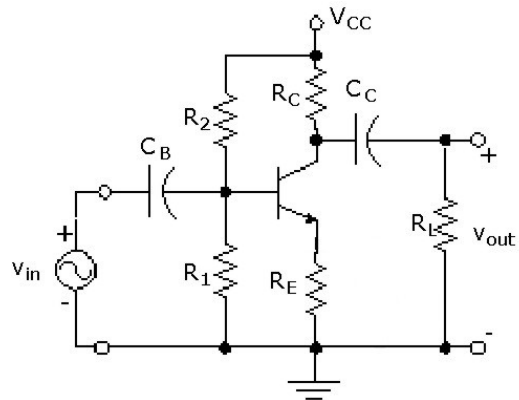
2. (25 pts) Given $R_C=R_L=2k\Omega$, $R_E=200\Omega$, $\beta=200$, $V_{BE}=0.7V$, $V_{CC}=15V$ and all capacitors are infinite and ideal:
 - a. select R_1 and R_2 for maximum possible symmetric current swing;
 - b. determine the maximum symmetrical output voltage swing.



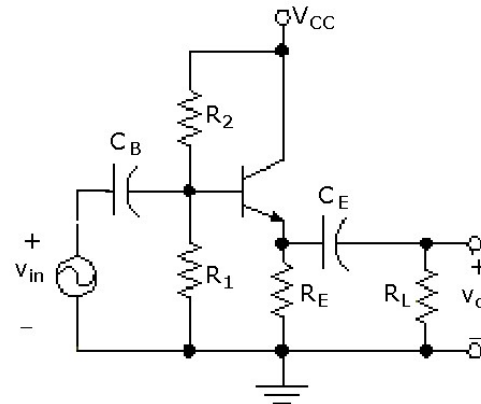3. (35 pts) Given $R_1=8k\Omega$, $R_2=2k\Omega$, $R_E=R_L=1k\Omega$, $\beta=80$, $V_{BE}=0.7V$ and $V_{CC}=15V$:
 - a. determine the maximum symmetrical output voltage swing ;
 - b. sketch the ac & dc load lines;
 - c. calculate the conversion efficiency of the amplifier.




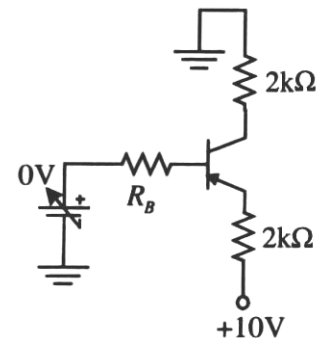Extra Credit: (25 points max) For the circuit to the right, determine the β of the transistor at saturation when $R_B=100k\Omega$, $V_{BE} = -0.7V$ and $V_{CE(sat)} = -0.2V$.



P1

Ex 4.2, p169

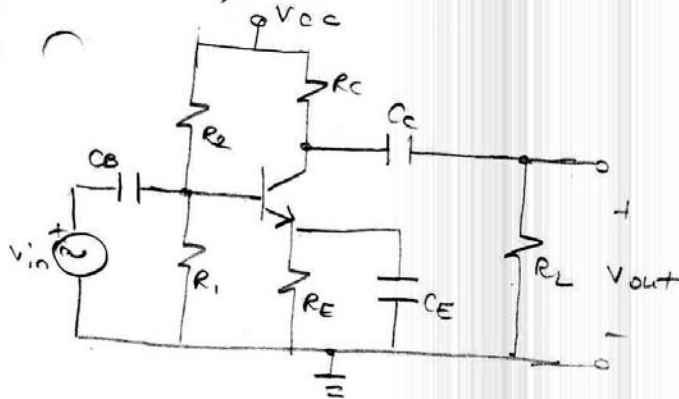

Given:

1/2

$$R_1 = 1.5 \text{ k}\Omega$$

$$R_2 = 7 \text{ k}\Omega$$

$$R_E = 100 \Omega$$

$$R_C = R_L = 1 \text{ k}\Omega$$

$$\beta = 180$$

$$V_{BE} = 0.7 \text{ V}$$

$$V_{CC} = 5 \text{ V}$$

caps: $\infty + \text{ideal}$

(w: perfect open to dc, perfect short to ac)

$$\Rightarrow I_{CQ} = \frac{V_{BB} - V_{BE}}{R_B/\beta + R_E}$$

$$2 \quad V_{BB} = \frac{R_2 V_{CC}}{R_1 + R_2} = \frac{(1.5 \text{ k})(5)}{1.5 \text{ k} + 7 \text{ k}} = 0.882 \text{ V}$$

$$2 \quad R_B = R_1 \parallel R_2 = (1.5 \text{ k}) \parallel (7 \text{ k}) = 1.24 \text{ k}\Omega$$

$$3 \quad I_{CQ} = \frac{0.882 - 0.7}{1.24 \text{ k}/180 + 100} = \underline{1.70 \text{ mA}}$$

$$3 \quad V_{CEQ} = V_{CC} - I_{CQ} R_{DC} = V_{CC} - I_{CQ} (R_C + R_E) \\ = 5 - (1.7 \times 10^{-3})(1000 + 100) = \underline{3.13 \text{ V}}$$

$$b) \quad 2 \quad V_{CC} = V_{CEQ} + I_{CQ} R_{AC} = V_{CEQ} + I_{CQ} (R_C \parallel R_L) \\ = 3.13 + (1.7 \text{ m})(0.5 \text{ k}) = 3.98 \text{ V}$$

$$2 \quad I_{CC} = \frac{V_{CC}}{R_{AC}} = \frac{3.98}{500} = 7.96 \text{ mA}$$

3 $I_{CQ} < \frac{I_{CC}}{2}$ \therefore Q-pt in lower half of load line

$$3 \quad V_{opp} = 2(I_{CQ} - 0)(R_C \parallel R_L) = 2(1.7 \text{ m})(0.5 \text{ k}) = \underline{1.7 \text{ V}_{pp}}$$

P1 (cont)

2/2

$$c) P_{out(ac)} = \frac{1}{2} i_L^2 R_L$$

4 since $R_L = R_C$, $i_L = \frac{1}{2} I_{OQ}$ (current division)


$$b) P_{out(ac)} = \frac{1}{2} \left(\frac{1.7 \times 10^{-3}}{2} \right)^2 (10^3) = 0.361 \times 10^{-3} \text{ W} = \underline{361.4 \mu\text{W}}$$

$$d) P_{V_{ce}(dc)} = I_{OQ} V_{ce} + \frac{V_{cc}^2}{R_1 + R_2} = (1.7 \times 10^{-3})(5) + \frac{5^2}{(1.5+7) \times 10^3}$$

$$\rightarrow = 8.5 \text{ m} + 2.94 \text{ m} = \underline{11.44 \text{ mW}}$$

P2)

Ex 4.2 + 4.3

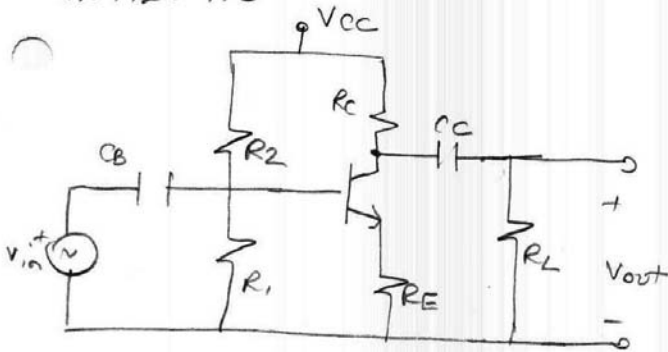

Given:

$$V_{CC} = 15V$$

$$V_{BE} = 0.7V$$

$$R_C = R_L = 2k\Omega$$

$$R_E = 200\Omega$$

$$\beta = 200$$

a) max swing \Rightarrow Q-pt in center of load line

$$2) R_{oc} = R_C \parallel R_L + R_E = 2k \parallel 2k + 200 = 1.2k\Omega$$

$$2) R_{dc} = R_C + R_E = 2k + 200 = 2.2k\Omega$$

$$4) I_{CQ} = \frac{V_{CC}}{R_{oc} + R_{dc}} = \frac{15}{1.2k + 2.2k} = 4.41mA$$

$$3) \text{ Let: } R_B = 0.1\beta R_E = 0.1(200)(200) = 4k\Omega$$

$$3) V_{BB} = V_{BE} + I_{CQ}(R_B/\beta + R_E) = 0.7 + (4.41 \times 10^{-3})\left(\frac{4000}{200} + 200\right) = 1.67V$$


$$3) R_1 = \frac{R_B}{1 - V_{BB}/V_{CC}} = \frac{4k}{1 - 1.67/15} = 4.5k\Omega$$

$$3) R_2 = \frac{V_{CC}R_B}{V_{BB}} = \frac{(15)(4k)}{1.67} = 35.9k\Omega$$

b) Q-pt in center

$$5) V_{opp} = 2I_{CQ}(R_L \parallel R_C) = 2(4.41mA)(2k \parallel 2k) = 8.82V_{pp}$$

Ex. 7

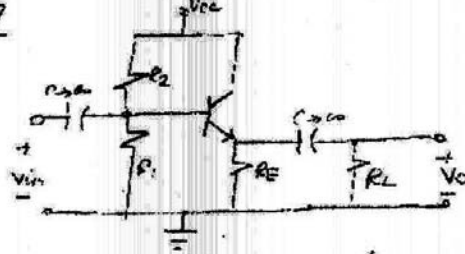

- $V_{CC} = 15V$
- $R_1 = 8k\Omega$
- $R_2 = 2k\Omega$
- $R_E = 1k\Omega$
- $R_L = 1k\Omega$
- $V_{BE} = 0.7V$
- $\beta = 80$

max symmetric voltage swing ($V_{osymp-p}$) = ?

$$V_{BB} = \frac{R_2 V_{CC}}{R_1 + R_2} = \frac{(2k)(15)}{8k + 2k} = 12V$$

$$R_B = R_1 || R_2 = (8k) || (2k) = 1.6k\Omega$$

$$I_{CQ} = \frac{V_{BB} - V_{BE}}{\frac{R_B}{\beta} + R_E} = \frac{12 - 0.7}{\frac{(1.6k)\Omega}{80} + 1k} = 1.108 \times 10^{-2} A = 11.08 mA$$

*cannot assume this is in the center of the load line, so must solve for I_{CQ} (use $I_E = I_C$)


$$V_{CEQ} = V_{CC} - I_{CQ} R_E = 15 - (11.08 \times 10^{-3})(1k) = 3.92V$$

$$V_{CC} = V_{CEQ} + I_{CQ} (R_E || R_L) = 3.92 + (11.08 \times 10^{-3})(1k || 1k) = 9.46V$$

$$I_{CC} = \frac{V_{CC}}{R_E || R_L} = \frac{9.46}{500} = 18.92 mA$$

$$V_{osymp-p} = 2(I_{CC} - I_{CQ})(R_E || R_L) = 2(18.92 - 11.08)(10^{-3})(500)$$

$$V_{osymp-p} = 7.84 V_{pp}$$

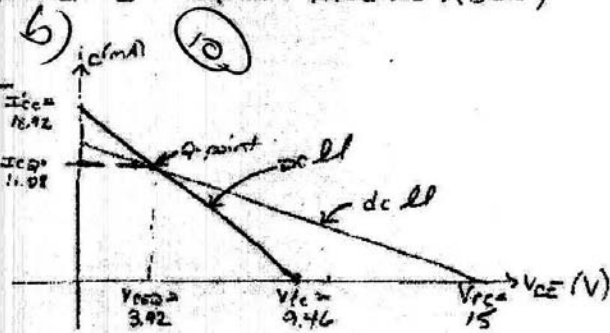

$$c) \eta = \frac{P_{out(ac)}}{P_{in(dc)}} \times 100$$

P3 (cont)

$$R_2 = R_E \quad \therefore i_L = \frac{1}{2} I_{CQ} = \frac{11.08 \text{ mA}}{2}$$

$$P_{out(ac)} = \frac{1}{2} i_L^2 R_L = \frac{1}{2} \left(\frac{I_{CQ}}{2} \right)^2 R_L = \frac{I_{CQ}^2 R_L}{8}$$


$$P_{out(ac)} = \frac{(11.08 \times 10^{-3})^2 (10^3)}{8} = 15.35 \text{ mW}$$

$$P_{in(dc)} = V_{CEQ} I_{CQ} + I_{CQ}^2 R_E + \frac{V_{CC}^2}{R_1 + R_2}$$

$$= (3.92)(11.08 \text{ mA}) + (11.08 \text{ mA})^2 (1 \text{ k}) + \frac{15^2}{10 \text{ k}} =$$

$$P_{in(dc)} = 43.43 \text{ m} + 122.77 \text{ m} + 22.5 \text{ m} = 188.73 \text{ mW}$$
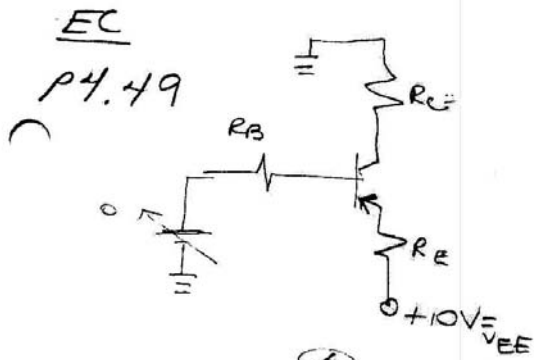
$$\eta = \frac{15.35 \text{ m}}{188.73 \text{ m}} \times 100 = \underline{8.13\%}$$



Given:
 $R_B = 100\text{ k}\Omega$ $R_C = R_E = 2\text{ k}\Omega$

$$V_{CE(\text{sat})} = -0.2\text{ V}$$

$$V_{BE} = -0.7\text{ V}$$

$$\beta = 100$$

want: β of transistor at saturation

⑥
 w/ value of β given: $I_C = \frac{-V_{EE} - V_{BE}}{\frac{R_B}{\beta} + R_E} = \frac{-10 - (-0.7)}{\frac{100\text{ k}}{100} + 2\text{ k}} = -3.1\text{ mA}$

⑦
 $I_{C(\text{sat})} = \frac{-V_{EE} - V_{CE(\text{sat})}}{R_C + R_E} = \frac{-10 - (-0.2)}{4\text{ k}} = -2.45\text{ mA}$

⑧
 $I_{C(\text{sat})} = \frac{-V_{EE} - V_{BE}}{\frac{R_B}{\beta} + R_E}$, everything known but β

$$I_{C(\text{sat})} \left(\frac{R_B}{\beta} + R_E \right) = -V_{EE} - V_{BE}$$

$$\frac{R_B}{\beta} = \frac{-V_{EE} - V_{BE} - I_{C(\text{sat})} R_E}{I_{C(\text{sat})}}$$

⑨ $\beta = \frac{I_{C(\text{sat})} R_B}{-V_{EE} - V_{BE} - I_{C(\text{sat})} R_E}$

$$\beta = \frac{(-2.45 \times 10^{-3})(100 \times 10^3)}{-10 - (-0.7) - (-2.45 \times 10^{-3})(2 \times 10^3)} = \frac{-245}{-4.4} = \underline{55.7}$$