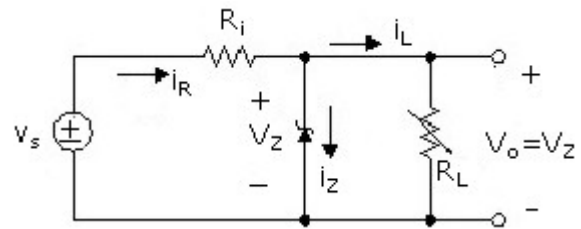



Show all work. Clearly indicate final answer(s).

- (20 pts) A particular diode has a reverse saturation current of $0.2\mu\text{A}$ and $n=1.6$. Determine the diode current when the voltage across the diode is 0.4V . Also determine the forward resistance of the diode at this operating point. Use $V_T=26\text{mV}$.
- (20 pts) A half-wave rectifier output has 50V amplitude at 60Hz . Assuming no forward resistance in the diode, what minimum load could be added to the circuit when using a $50\mu\text{F}$ capacitor to maintain the voltage above 40V ?

- (30 pts) A Zener diode regulator circuit has an input whose voltage varies between 10V and 15V , and a load whose current varies between 100mA and 500mA . Find
 - the values of R_i and $I_{Z\text{max}}$ assuming that a 6-volt Zener is used.
 - the power ratings for the Zener diode and for the input resistor.




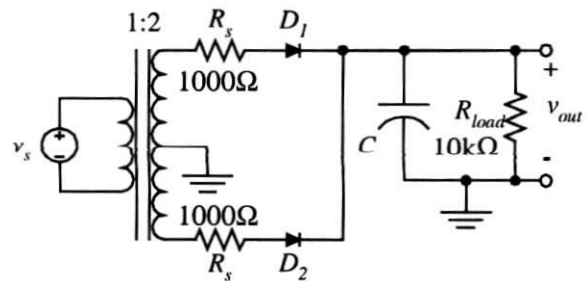
- (30 pts) If the output load of a full-wave rectifier is $10\text{k}\Omega$, what value of capacitor is required to maintain an output voltage that will not vary more than 10% ? The input is 120Vrms at 60Hz . Draw the output waveform. Consider the diodes and transformer idea.



Extra Credit: (25 points max)

The signal shown with a frequency of 5kHz is applied to the circuit given to the right, with the values $R_S=0$, $R=10\text{k}\Omega$, $C=0.5\mu\text{F}$, $R_F=0$, $R_r \rightarrow \infty$ and $V_{ON}=0$.

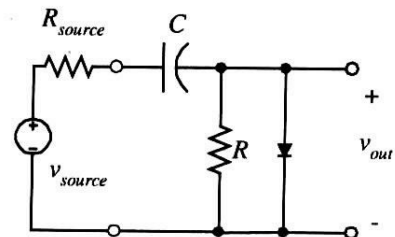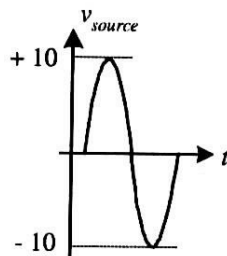- Sketch the output waveform, v_{out} .
- Repeat part (a) if $R=1\text{k}\Omega$ and $C=0.001\mu\text{F}$



T1E07


(3.11)
P1) given $I_0 = 0.2 \mu\text{A}$
 $n = 1.6$
 $V_T = 26 \text{ mV}$

want: I_D when $v_D = 0.4 \text{ V}$
 R_F

use $I_D = I_0 (e^{v_D/nV_T} - 1)$; $R_F = \frac{nV_T}{I_D}$

$$I_D = (0.2 \times 10^{-6}) \left(e^{\frac{0.4}{(1.6)(0.026)}} - 1 \right) \approx 3 \times 10^{-3} \text{ A} = \underline{\underline{3 \text{ mA}}}$$

$$R_F = \frac{(1.6)(0.026)}{0.003} \approx \underline{\underline{13.9 \Omega}}$$

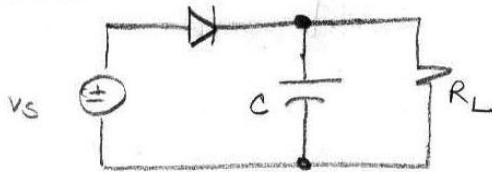E3.4Want: R_{Lmin} given: $v_s = 50V @ 60Hz$ ($R_L = R_f = 0$)

$$C = 50\mu F$$

$$V_{min} = 40V$$

$$\text{use (3.52)} \quad C = \frac{V_{max}}{\Delta V f_p R_L}$$

$$\text{to obtain: } R_L = \frac{V_{max}}{\Delta V f_p C}$$


where $V_{max} = 50V$

$$\Delta V = 50 - 40 = 10V$$

 $f_p = 60Hz$ (half wave rectifier)

$$R_{Lmin} = \frac{50}{(10)(60)(50 \times 10^{-6})} \approx 1.67 \times 10^3 \Omega$$

$$\underline{\underline{R_{Lmin} = 1.67k\Omega}}$$

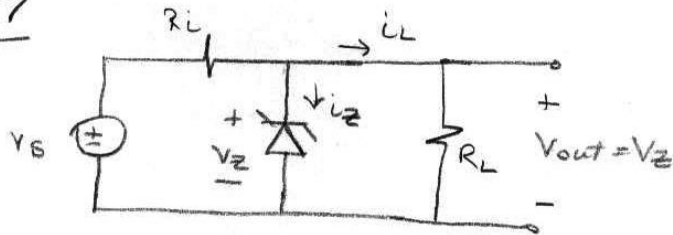E3.7want: $R_i + I_{Zmax}$ given: $V_{Smin} = 10V$ $V_{Smax} = 15V$ $I_{Lmin} = 100mA$ $I_{Lmax} = 500mA$ $V_Z = 6V$

$$\text{use (3.61): } I_{Zmax} = \frac{(0.100)(6-10) + (0.500)(15-6)}{10 - (0.9)(6) - (0.1)(15)}$$

$$I_{Zmax} = \frac{-0.4 + 4.5}{10 - 5.4 - 1.5}$$

$$\underline{\underline{I_{Zmax} = 1.32 A}}$$

$$\text{use (3.58) } R_i = \frac{V_{Smax} - V_Z}{I_{Lmin} + I_{Zmax}} = \frac{15 - 6}{0.100 + 1.32}$$

$$\underline{\underline{R_i = 6.34 \Omega}}$$

P3 (cont)

E3.8 from E3.7: $V_Z = 6V$, $I_{Zmax} = 1.32A$

$$R_i = 6.33\Omega$$

$$I_{rmax} = I_{Zmax} + I_{Lmin} = 1.42A$$


$$P_Z = V_Z I_{Zmax} = (6)(1.32) = \underline{\underline{7.92W}}$$

$$P_{ri} = I_{rmax}^2 R_i = (1.42)^2 (6.33) = \underline{\underline{12.76W}}$$

or

$$P_{ri} = V_{rmax} I_{rmax} = (15-6)(1.42) = \underline{\underline{12.78W}}$$

↖ close
↘ enough
~

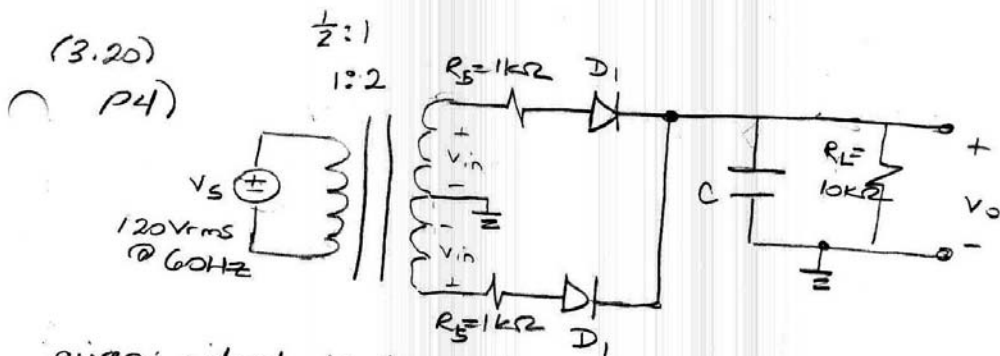


given: ideal diodes + transformer
 want: C so that $\Delta v_{out} \leq 10\%$

$$V_{in} = \frac{(120\sqrt{2})}{(2)(2)} = 169.7 \text{ V (max)}$$



$$V_o = \frac{(10k) V_{in}}{10k + 1k} = \frac{(10k)(169.7)}{11k} = 154.3 \text{ V (max) (voltage divider)}$$

$$(10\%) \Delta V_o = (0.1)(154.3) = 15.4 \text{ V}$$
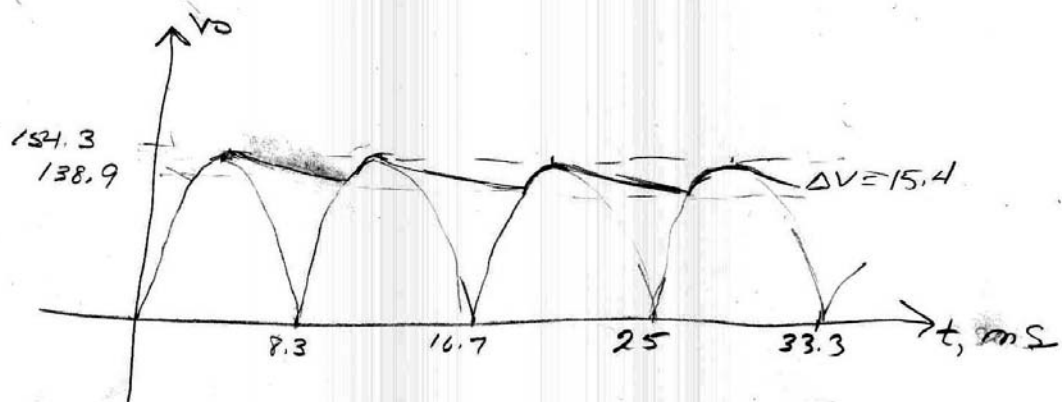
$$C = \frac{V_{max}}{\Delta V f_p R_L} = \frac{154.3}{(15.4)(120)(10k)} = \underline{\underline{8.35 \mu\text{F}}}$$



(p3.48)
EC

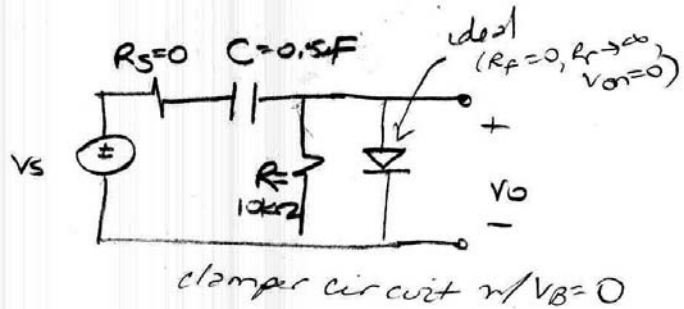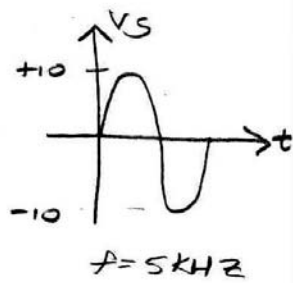

a) $v_o = ?$


b) $v_o = ?$ if $R = 1 \text{ k}\Omega + C = 0.001 \mu\text{F}$

Need $\tau \geq \frac{5T}{2}$, $\tau = RC$

$f = 5 \text{ kHz}$, $T = \frac{1}{f} = 200 \mu\text{s}$

$\tau_{\text{min}} = \frac{5(200 \mu\text{s})}{2} = 500 \mu\text{s}$

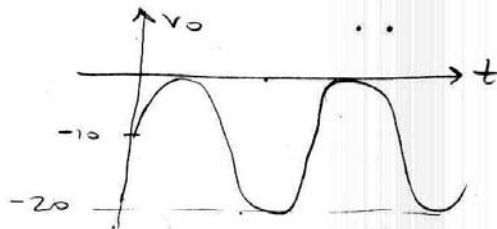a) $RC = (10 \times 10^3)(0.5 \times 10^{-6}) = 5000 \mu\text{s} > 500 \mu\text{s}$
acts like std clamper



b) $RC = (10^3)(0.001 \times 10^{-6}) = 1 \mu\text{s} < 500 \mu\text{s}$

* does not act as clamper, acts as half wave rectifier

