
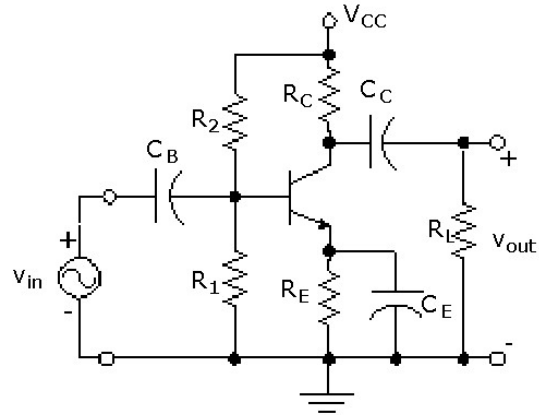


Show all work. Clearly indicate final answer(s).

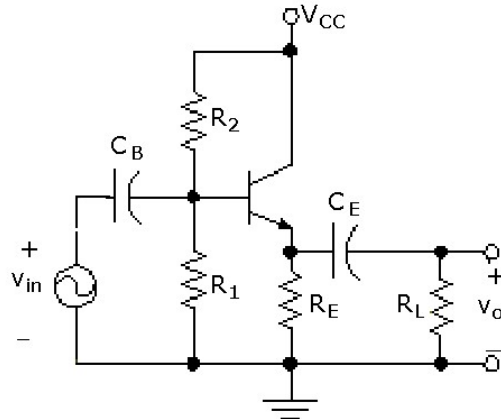
1. (20 pts) For the amplifier to the right, use the following values: $V_{CC}=20V$, $V_{BE}=0.7V$, $\beta=100$, $R_C=R_L=2k\Omega$, $R_E=200\Omega$, and all capacitors infinite and ideal. Find:
 - a. R_1 and R_2 for $I_{CQ}=8mA$
 - b. The symmetrical output voltage swing for the values of part (a)



2. (30 points) For the amplifier to the right, use the following values: $V_{CC}=12V$, $V_{BE}=0.7V$, $\beta=100$, $R_1=10k\Omega$, $R_2=20k\Omega$, $R_E=R_L=600\Omega$, and all capacitors infinite and ideal.
 - a. Determine the symmetrical output voltage swing.
 - b. Sketch the ac and dc load lines




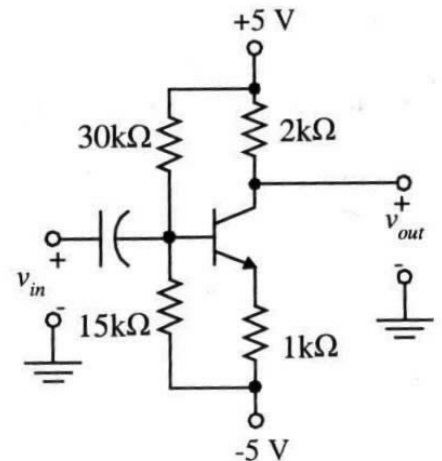3. (20 points) For the circuit shown to the right, determine the output voltage, v_{out} , when $V_{BE}=0.7V$, $\beta = 200$ and $v_{in}=0$.
4. (30 points) For the circuit of problem 1, use $V_{CC}=5V$, $V_{BE}=0.7V$, $\beta=180$, $R_C=R_L=1k\Omega$, $R_E=100\Omega$, and all capacitors infinite and ideal.
 - a. Select R_1 and R_2 for maximum output voltage swing
 - b. Determine V_{opp}
 - c. Calculate the maximum conversion efficiency η




Extra Credit: (25 points max) An ac voltage source v_{TH} is applied directly to the base of an npn transistor as shown in the figure to the right. The internal resistance of the ac source is shown as R_{source} .

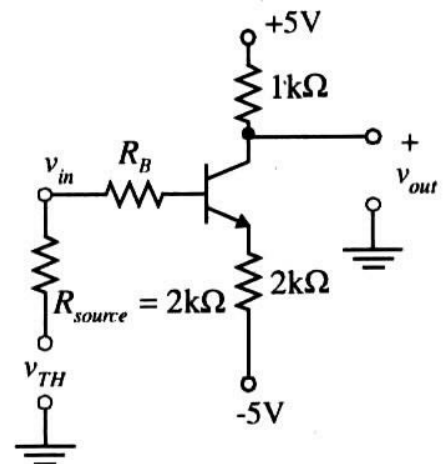- a. Determine I_{CQ} , V_{CEQ} , and V_{out} when the ac input is zero, assuming $\beta=100$, $V_{BE}=0.7V$ and $R_B=0$.
- b. What value of resistor needs to be added in the base circuit to make the output go to 3V when $v_{in}=0$?



P4.24

(1)

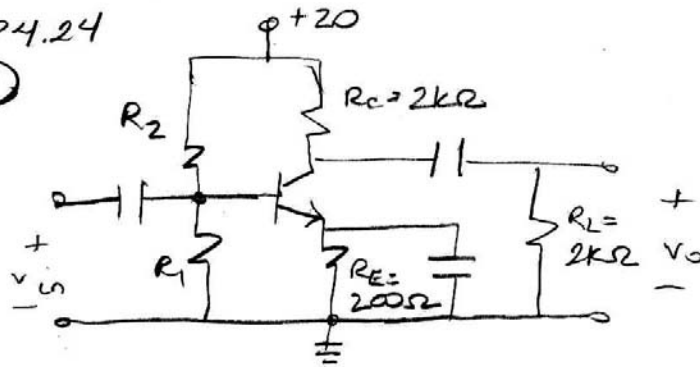

$$V_{BE} = 0.7V$$

$$\beta = 100$$

a) Given $I_{CQ} = 8mA$, find R_1 and R_2

$$R_1 = \frac{R_B}{1 - V_{BB}/V_{CC}} \quad R_2 = \frac{R_B V_{CC}}{V_{BB}}, \text{ need } R_B, V_{BB}$$

$$V_{BB} = V_{BE} + I_{CQ} \left(\frac{R_B}{\beta} + R_E \right), \text{ need } R_B$$

$$\text{Use } R_B = 0.1 \beta R_E = (0.1)(100)(200) = 2k\Omega$$

$$V_{BB} = 0.7 + (0.008) \left(\frac{2000}{100} + 200 \right) = 2.46V$$

$$R_1 = \frac{2k}{1 - 2.46/20} = 2.28k\Omega \quad R_2 = \frac{(2k)(20)}{2.46} = 16.26k\Omega$$

b) $V_{opp} = ?$

$$V_{CEQ} = V_{CC} - I_{CQ} R_{DC} = 20 - (8m)(2.2k) = 2.4V$$


$$V_{CC'} = V_{CEQ} + I_{CQ} R_{AC} = 2.4 + (8m)(1k) = 10.4V$$

$$I_{CC} = \frac{V_{CC'}}{R_{AC}} = \frac{10.4}{1k} = 10.4mA ; I_{CQ} > \frac{I_{CC}}{2} \therefore \text{Qpt in lower half}$$

$$V_{opp} = 2(I_{CC} - I_{CQ})R_{AC} = 2(10.4m - 8m)(1k) = 4.8V$$

Example 4.5

②

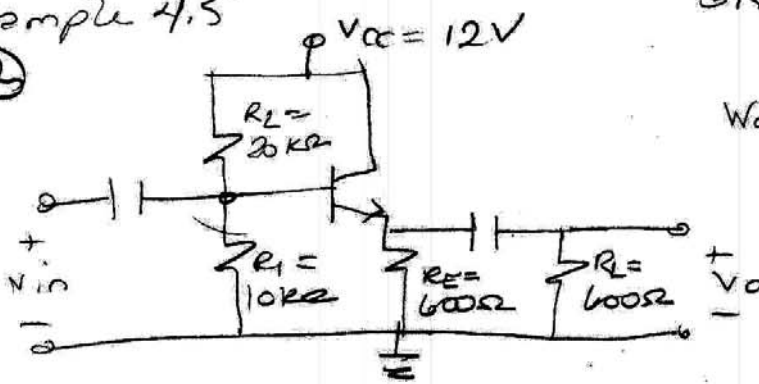

Given: $V_{BE} = 0.7V$
 $\beta = 100$

Want V_{opp}

$$R_B = R_1 \parallel R_2 = 10K \parallel 20K = 6.67K\Omega$$

$$V_{BB} = \frac{R_2 V_{CC}}{R_1 + R_2} = \frac{(10K)(12)}{10K + 20K} = 4V$$

$$I_{CQ} = \frac{V_{BB} - V_{BE}}{R_B/\beta + R_E} = \frac{4 - 0.7}{\frac{6.67K}{100} + 0.6K} = 4.95mA$$

$$V_{CEQ} = V_{CC} - I_{CQ} R_{AC} = 12 - (4.95m)(0.6K) = 9.03V$$


$$V_{CC}' = V_{CEQ} + I_{CQ} R_{AC} = 9.03 + (4.95m)(0.3K) \approx 10.52V$$

\uparrow
 $R_E \parallel R_L$

$$I_{C'c} = \frac{V_{CC}'}{R_{AC}} = \frac{10.52}{0.3K} = 35.1mA$$


$I_{CQ} < \frac{I_{C'c}}{2}$ \therefore Q pt in lower half
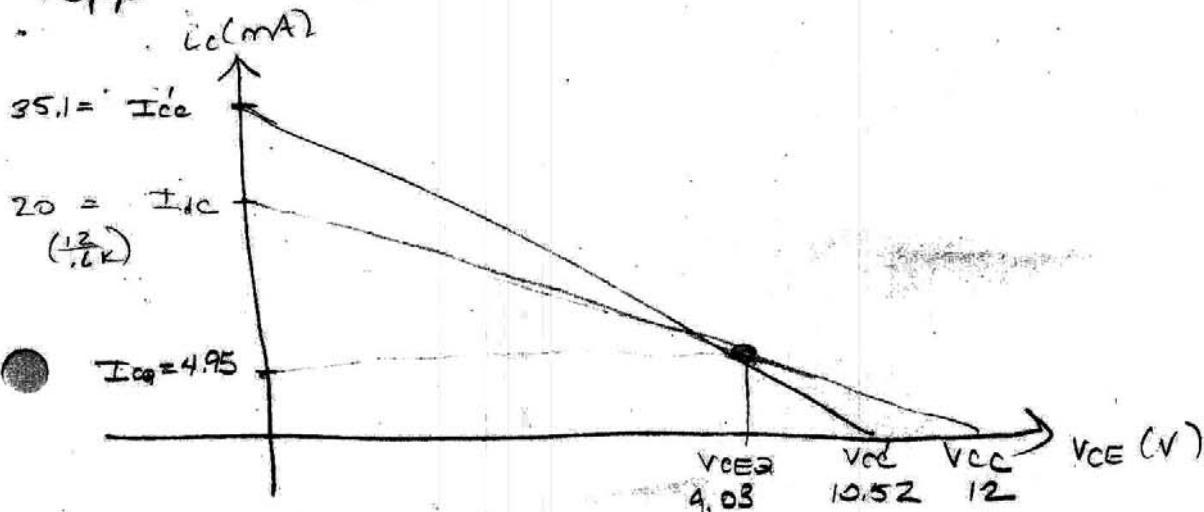
$$V_{opp} = 2(I_{CQ} - 0)R_{AC} = 2(4.95m)(0.3K) = \underline{\underline{2.97V}}$$



P 4.8

3

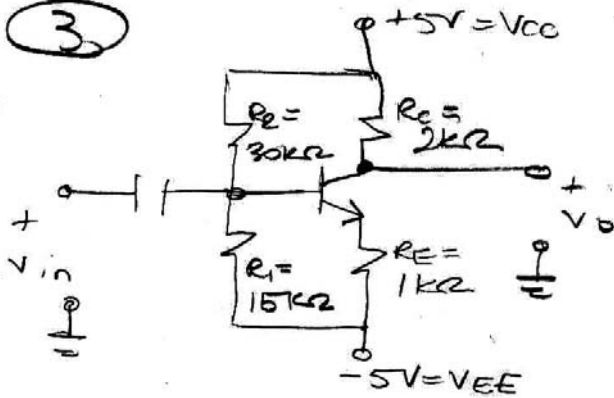

Given: $V_{BE} = 0.7V$
 $\beta = 200$
 $V_{in} = 0$

want: v_{out}

$$R_B = R_1 \parallel R_2 = (15K) \parallel (30K) = 10K\Omega$$


$$V_{BB} = \frac{R_2 (V_{CC} - V_{EE})}{R_1 + R_2} = \frac{(15K)(5 - (-5))}{30K + 15K} = 3.33V$$

$$I_{CQ} = \frac{V_{BB} - V_{BE}}{R_B/\beta + R_E} = \frac{3.33 - 0.7}{10K/200 + 1K} \approx 2.50mA$$

$$V_o = V_c = V_{CC} - I_{CQ} R_C = 5 - (2.5m)(2K) = \underline{0V}$$

Example 4.3

(4)

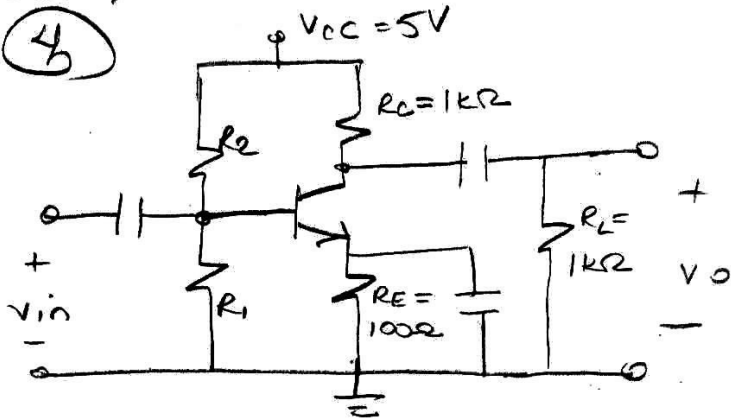

Given: $V_{BE} = 0.7V$
 $\beta = 180$

Want: max swing
 R_1, R_2, V_{app}, η

Let $R_B = 0.1 \beta R_E = (0.1)(180)(100) = 1.8k\Omega$

$$R_{ac} = R_C \parallel R_L = 1k \parallel 1k = 500\Omega$$

$$R_{dc} = R_C + R_E = 1k + 100 = 1.1k\Omega$$

$$I_{CQ} = \frac{V_{CC}}{R_{ac} + R_{dc}} = \frac{5}{1.6k} \approx 3.13mA$$

$$V_{BB} = V_{BE} + I_{CQ} \left(\frac{R_B}{\beta} + R_E \right) = 0.7 + (3.13m) \left(\frac{1.8k}{180} + 0.1k \right) = 1.04V$$

$$R_1 = \frac{R_B}{1 - V_{BB}/V_{CC}} = \frac{1.8k}{1 - 1.04/5} = 2.27k\Omega \quad R_2 = \frac{R_B V_{CC}}{V_{BB}} = \frac{(1.8k)(5)}{1.04} = 8.65k\Omega$$

$$V_{app} = 2 I_{CQ} R_{ac} = 2 (3.13m)(0.5k) = 3.13V$$

$$\eta = \frac{P_{out(ac)}}{P_{vcc(dc)}} \times 100 =$$

$$P_{vcc(dc)} = \frac{V_{CC}^2}{R_1 + R_2} + I_{CQ}^2 (R_C + R_E) + V_{CEQ} I_{CQ}$$

$$V_{CEQ} = V_{CC} - I_{CQ} R_{dc} = 5 - (3.13m)(1.1k) = 1.56V$$


$$P_{vcc(dc)} = \frac{5^2}{10.92k} + (3.13m)^2 (1.1k) + (1.56)(3.13m) = 17.95mW$$

$$P_{out(ac)} = \left(\frac{I_{CQ}}{2} \right)^2 R_{ac} = \left(\frac{3.13m}{2} \right)^2 (0.5k) = 1.22mW$$

$$\eta = \frac{1.22}{17.95} \times 100 \approx \underline{\underline{6.8\%}}$$

EC

P4.33+4.35

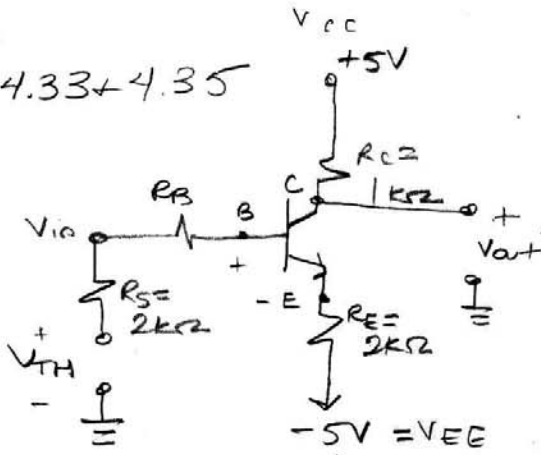

Given: $\beta = 100$
 $V_{BE} = 0.7V$
 $R_B = 0$
 $V_{TH} = 0$

Want I_{CQ}, V_{CEQ}, V_{out}

b) want R_B to make $V_{out} = 3V$

Not std bias ckt, so can't use std eqns

a) KVL @ BE loop @ Qpt

$$-V_{TH} + R_S I_{CQ} + R_B I_B + V_{BE} + I_E R_E + V_{EE} = 0$$

\downarrow $\frac{I_{CQ}}{\beta}$ \downarrow I_{CQ}

$$2k \left(\frac{I_{CQ}}{100} \right) + 0.7 + (2k) I_{CQ} + (-5) = 0$$

$$I_{CQ} (2020) = 4.3 ; I_{CQ} = \frac{4.3}{2020} \approx \underline{\underline{2.13mA}}$$

$$V_{CEQ} = (V_{CC} - V_{EE}) - I_{CQ} R_{DC} = 10 - (2.13m)(3k) = \underline{\underline{3.61V}}$$

$$V_o = V_c = V_{CC} - I_{CQ} R_C = 5 - (2.13m)(1k) = \underline{\underline{2.87V}}$$

b) work backwards (more or less)

$$V_o = V_{CC} - I_{CQ} R_C ; 3 = 5 - I_{CQ} (1k) ; I_{CQ} = \frac{5-3}{1k} = 2mA$$

from derived eqn w/ $R_B \neq 0$

$$\frac{R_S I_{CQ}}{\beta} + R_B \frac{I_{CQ}}{\beta} + V_{BE} + R_E I_{CQ} + V_{EE} = 0$$

$$\frac{(2k)(2m)}{100} + R_B \left(\frac{2m}{100} \right) + 0.7 + (2k)(2m) + (-5) = 0$$

$$R_B \left(\frac{0.002}{100} \right) - 0.26 = 0$$

$$R_B = 0.26 \left(\frac{100}{0.002} \right) = \underline{\underline{13k\Omega}}$$